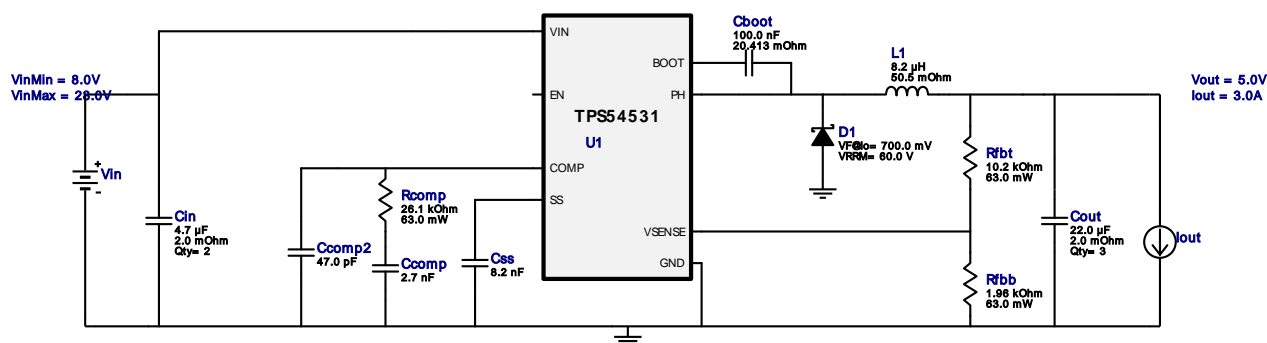



WEBENCH® Design Report

Design : 1231947/67 TPS54531DDAR
TPS54531DDAR 8.0V-28.0V to 5.00V @ 3.0A




Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	TDK	C1005X5R1A104K Series= X5R	Cap= 100.0 nF ESR= 20.413 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Ccomp	Yageo America	CC0805KRX7R9BB272 Series= X7R	Cap= 2.7 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	Ccomp2	Kemet	C0805C470K5GACTU Series= C0G	Cap= 47.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
4.	Cin	MuRata	GRM32ER71H475KA88L Series= X7R	Cap= 4.7 uF ESR= 2.0 mOhm VDC= 50.0 V IRMS= 5.35 A	2	\$0.31	 1210 15 mm ²
5.	Cout	MuRata	GRM32ER61E226KE15L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.67 A	3	\$0.28	 1210 15 mm ²
6.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
7.	D1	Diodes Inc.	B560C-13-F	VF@Io= 700.0 mV VRRM= 60.0 V	1	\$0.19	 SMC 83 mm ²
8.	L1	Bourns	SRP6540-8R2M	L= 8.2 uH DCR= 50.5 mOhm	1	\$0.49	 SRP6540 83 mm ²
9.	Rcomp	Vishay-Dale	CRCW040226K1FKED Series= CRCW..e3	Res= 26.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	Rfbb	Vishay-Dale	CRCW04021K96FKED Series= CRCW..e3	Res= 1.96 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	Rfht	Vishay-Dale	CRCW040210K2FKED Series= CRCW..e3	Res= 10.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
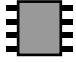
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	U1	Texas Instruments	TPS54531DDAR	Switcher	1	\$0.75	 DDA0008E 57 mm ²


IC Tj

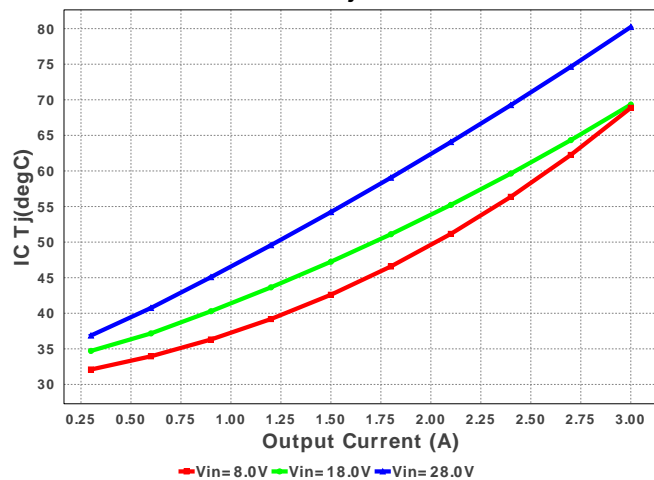


Duty Cycle

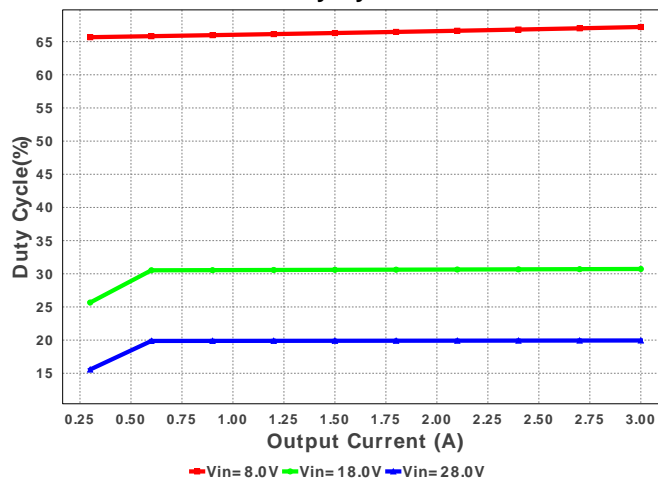


Cin IRMS

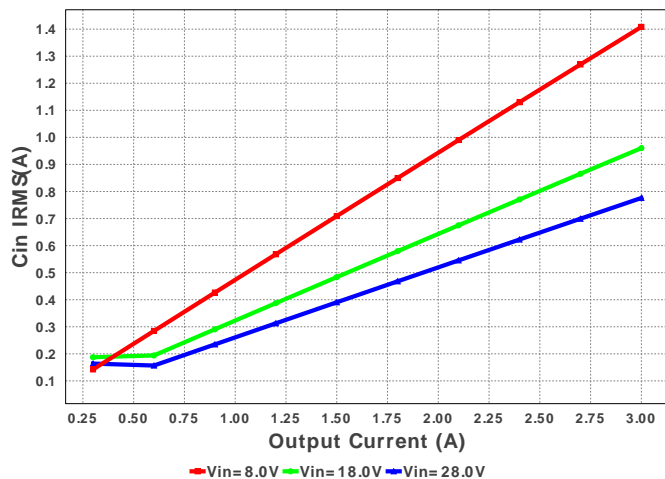


IC Ipk






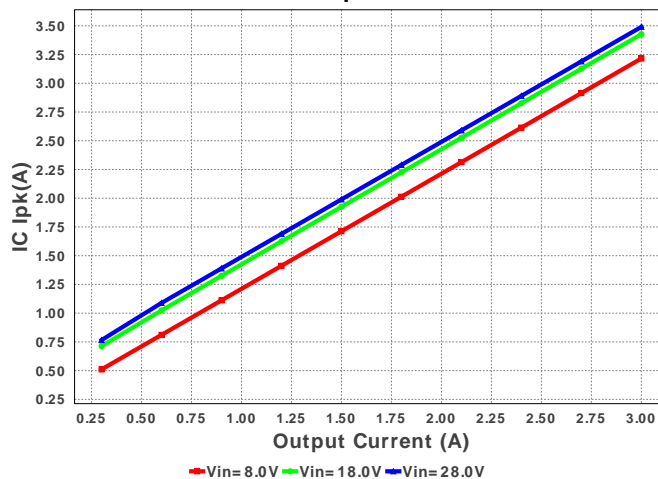








L Pd




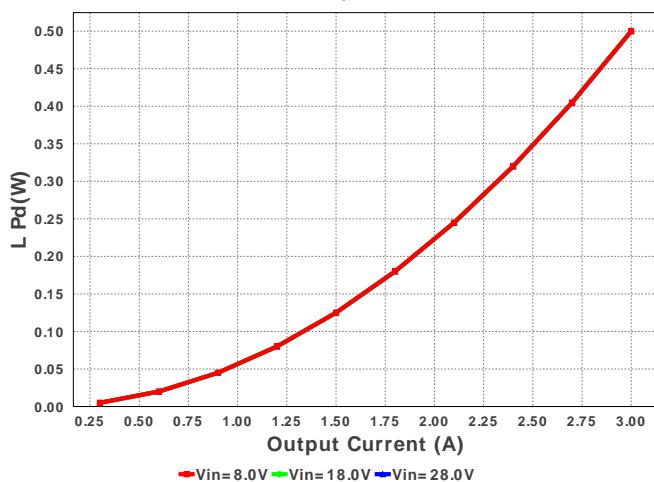


Low Freq Gain

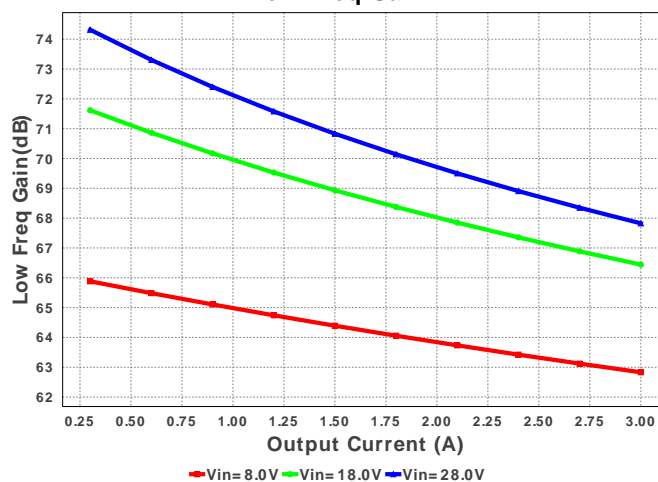

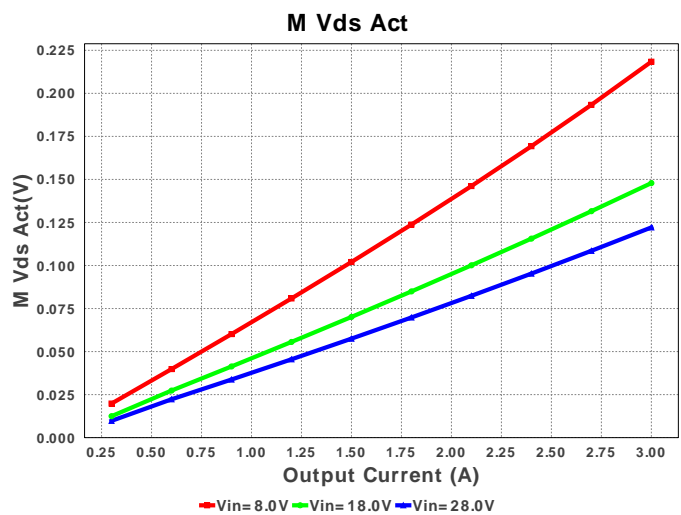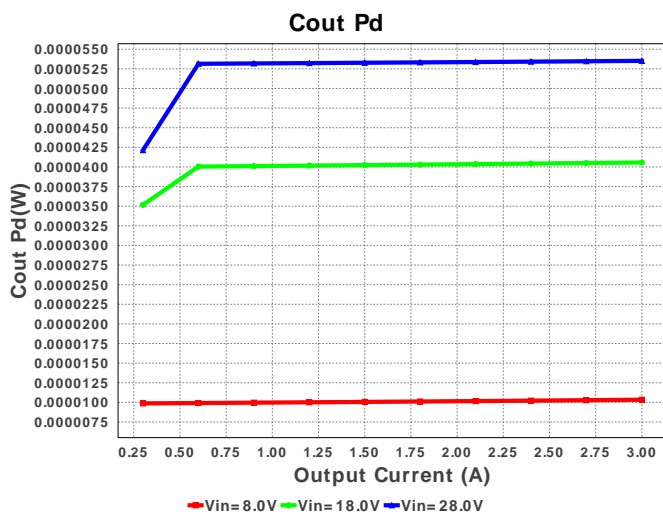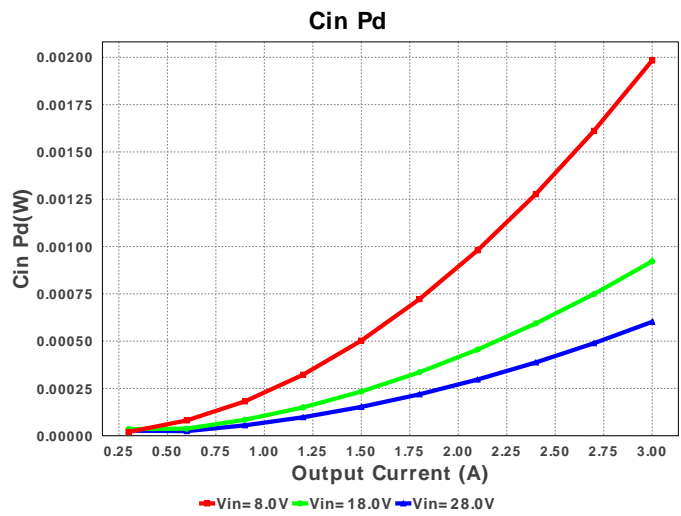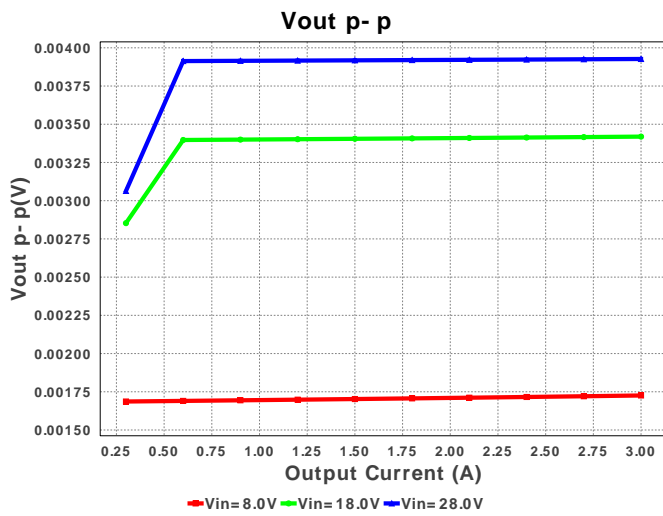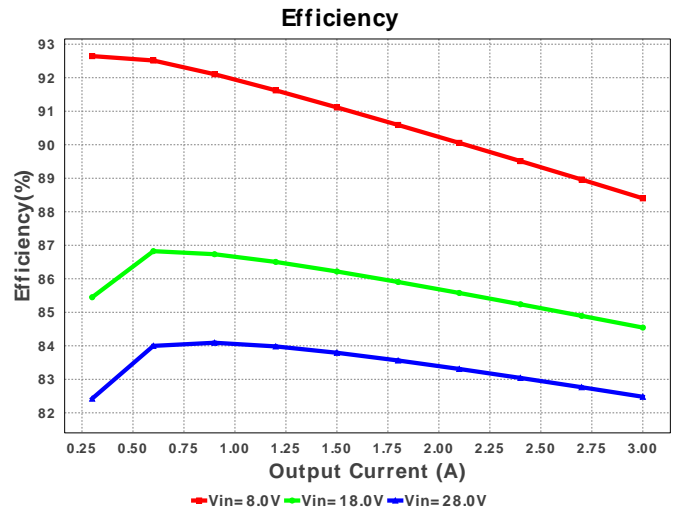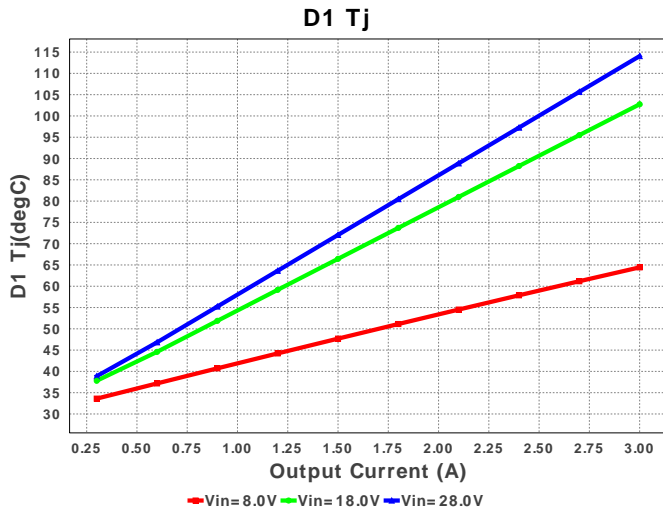

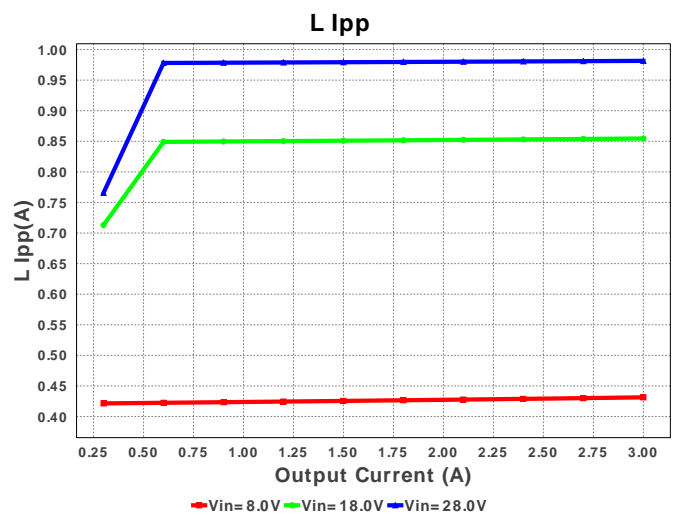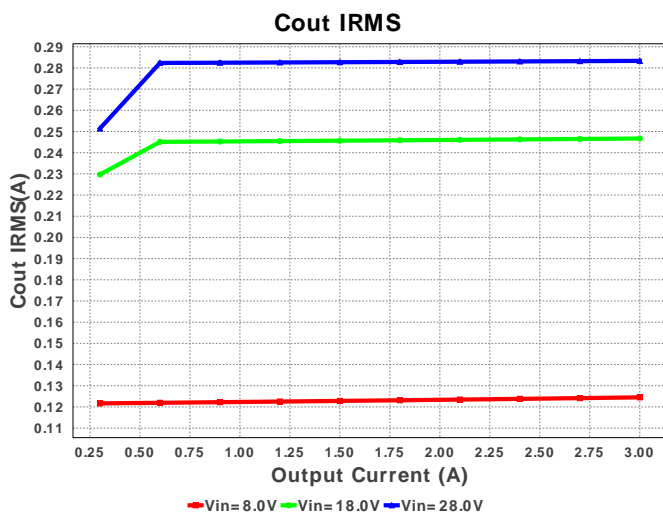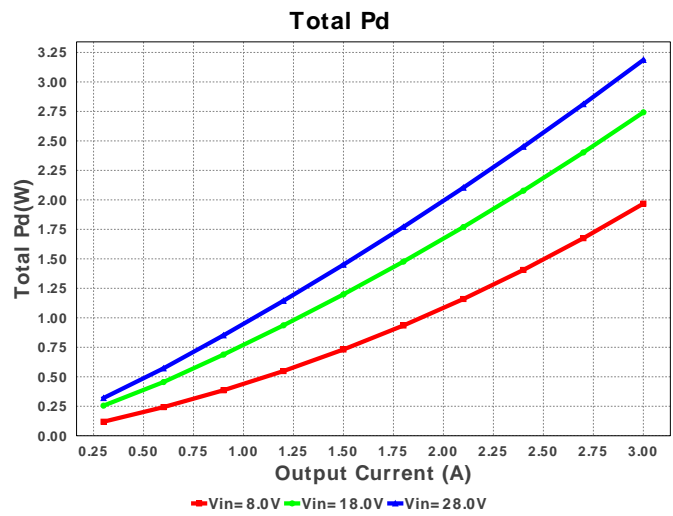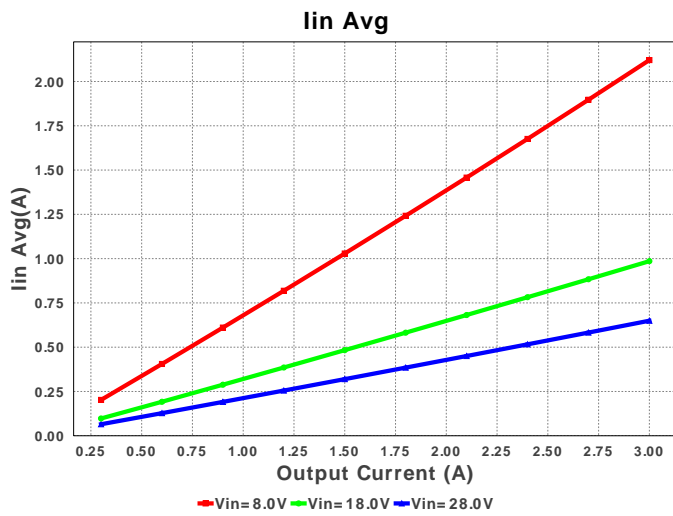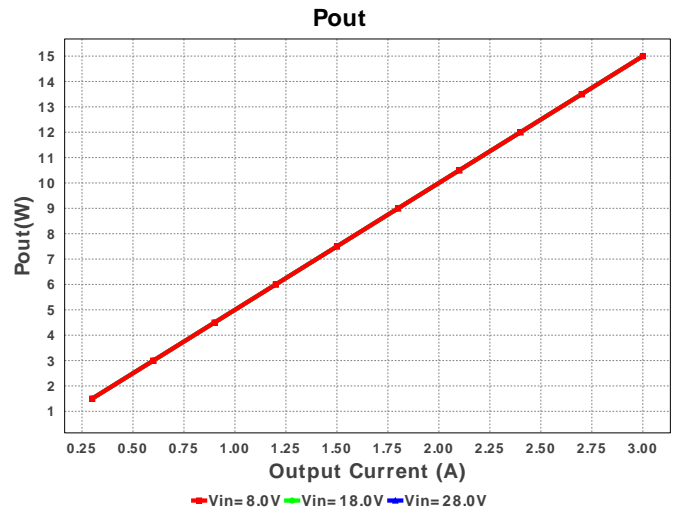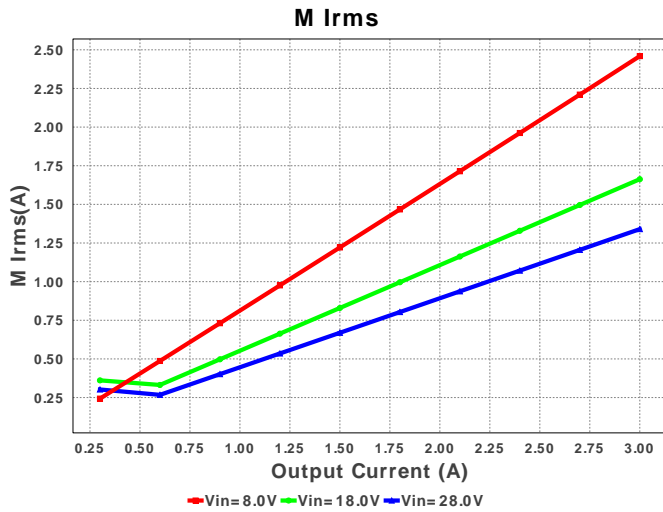

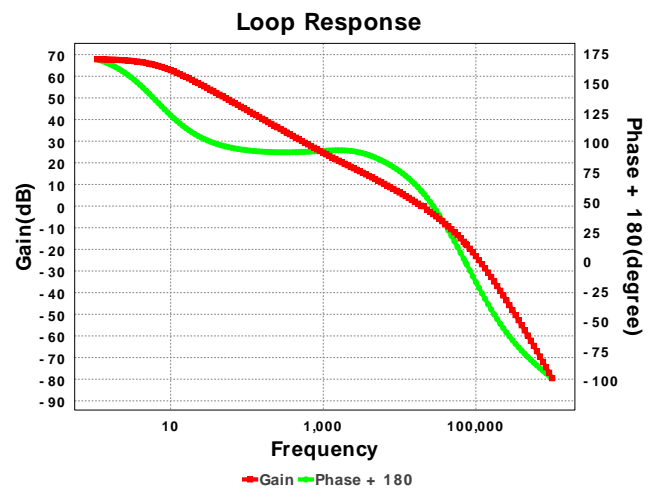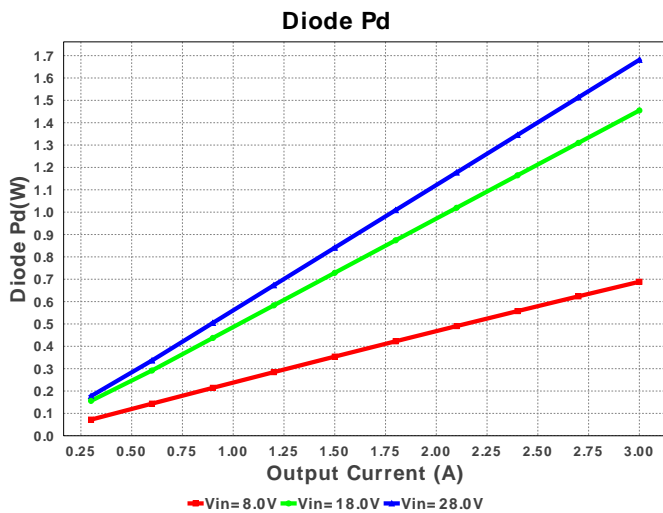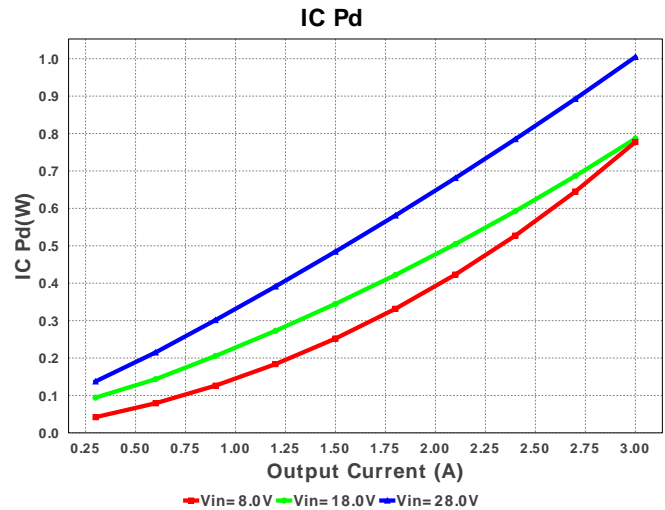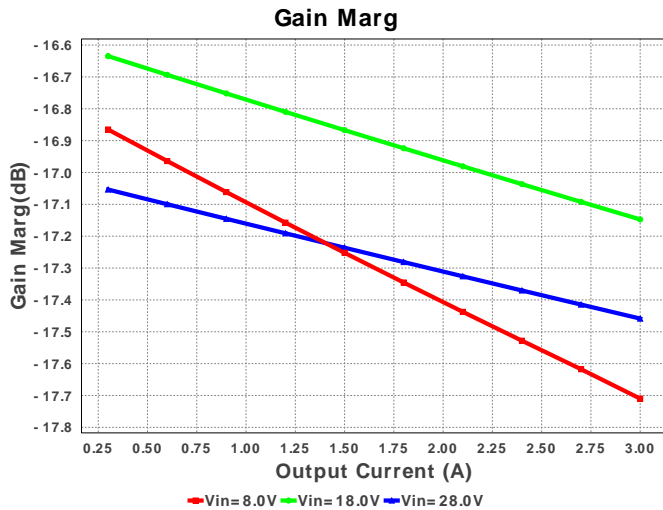

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	776.051 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	283.33 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	3.491 A	Current	Peak switch current in IC
4.	Iin Avg	649.52 mA	Current	Average input current
5.	L Ipp	981.49 mA	Current	Peak-to-peak inductor ripple current
6.	M1 Irms	1.34 A	Current	Q lavg
7.	BOM Count	15	General	Total Design BOM count
8.	FootPrint	324.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	570.0 kHz	General	Switching frequency
10.	M Vds Act	122.113 mV	General	Voltage drop across the MosFET
11.	Pout	15.0 W	General	Total output power
12.	Total BOM	\$2.96	General	Total BOM Cost
13.	D1 Tj	114.057 degC	Op_point	D1 junction temperature
14.	Vout OP	5.0 V	Op_point	Operational Output Voltage
15.	Cross Freq	19.489 kHz	Op_point	Bode plot crossover frequency
16.	Duty Cycle	19.945 %	Op_point	Duty cycle
17.	Efficiency	82.479 %	Op_point	Steady state efficiency
18.	Gain Marg	-18.104 dB	Op_point	Bode Plot Gain Margin
19.	IC Tj	80.229 degC	Op_point	IC junction temperature
20.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	3.0 A	Op_point	Iout operating point
22.	Phase Marg	60.185 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	28.0 V	Op_point	Vin operating point
24.	Vout p-p	4.341 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	602.255 μW	Power	Input capacitor power dissipation
26.	Cout Pd	160.552 μW	Power	Output capacitor power dissipation
27.	Diode Pd	1.681 W	Power	Diode power dissipation
28.	IC Pd	1.005 W	Power	IC power dissipation
29.	L Pd	499.95 mW	Power	Inductor power dissipation
30.	Total Pd	3.186 W	Power	Total Power Dissipation
31.	Low Freq Gain	67.825 dB	Unknown	Gain at 10Hz

Design Inputs

#	Name	Value	Description
1.	Iout	3.0	Maximum Output Current
2.	Iout1	3.0	Output Current #1
3.	VinMax	28.0	Maximum input voltage
4.	VinMin	8.0	Minimum input voltage
5.	Vout	5.0	Output Voltage
6.	Vout1	5.0	Output Voltage #1
7.	base_pn	TPS54531	Base Product Number
8.	source	DC	Input Source Type
9.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54531** Product Folder : <http://www.ti.com/product/tps54531> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).