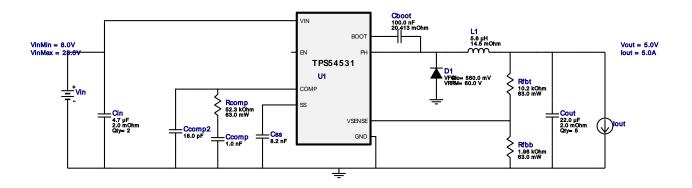


WEBENCH® Design Report

VinMin = 8.0V VinMax = 28.0V Vout = 5.0V Iout = 5.0A Device = TPS54531DDAR Topology = Buck Created = 3/27/15 4:00:56 PM BOM Cost = \$4.26 Footprint = 309.0 mm² BOM Count = 17 Total Pd = 4.51W

Design: 1231947/66 TPS54531DDAR TPS54531DDAR 8.0V-28.0V to 5.00V @ 5.0A





Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	TDK	C1005X5R1A104K Series= X5R	Cap= 100.0 nF ESR= 20.413 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Ccomp	Yageo America	CC0805JRNPO9BN102 Series= C0G	Cap= 1.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
3.	Ccomp2	Kemet	C0805C180K5GACTU Series= C0G	Cap= 18.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	MuRata	GRM32ER71H475KA88L Series= X7R	Cap= 4.7 uF ESR= 2.0 mOhm VDC= 50.0 V IRMS= 5.35 A	2	\$0.31	1210 15 mm ²
5.	Cout	MuRata	GRM32ER61E226KE15L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.67 A	5	\$0.28	1210 15 mm ²
6.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
7.	D1	Diodes Inc.	PDS760-13	VF@Io= 560.0 mV VRRM= 60.0 V	1	\$0.60	PowerDI5 50 mm ²
8.	L1	Coilcraft	XAL6060-562MEB	L= 5.6 μH DCR= 14.5 mOhm	1	\$0.82	XAL6060 72 mm ²
9.	Rcomp	Vishay-Dale	CRCW040252K3FKED Series= CRCWe3	Res= 52.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
10.	Rfbb	Vishay-Dale	CRCW04021K96FKED Series= CRCWe3	Res= 1.96 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
11.	Rfbt	Vishay-Dale	CRCW040210K2FKED Series= CRCWe3	Res= 10.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²


Name Manufacturer Part Number Properties Qty Price Footprint

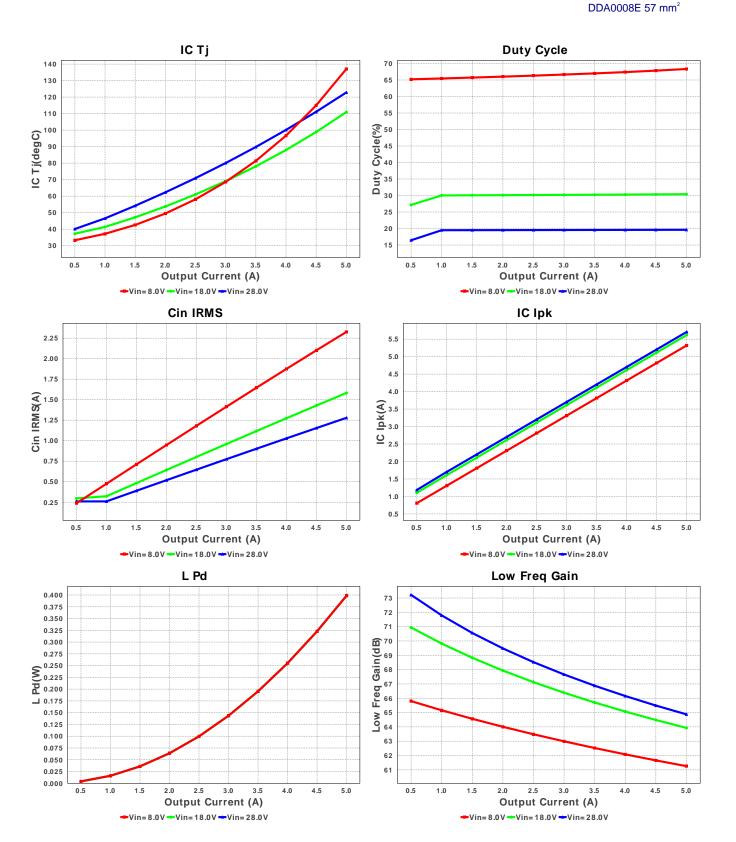12. U1 Texas Instruments TPS54531DDAR Switcher 1 \$0.75



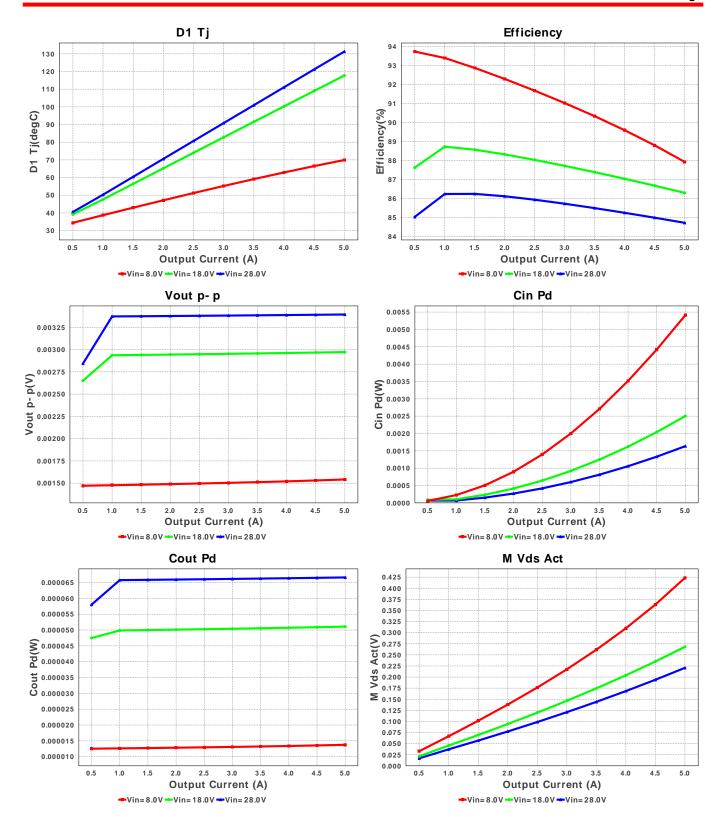

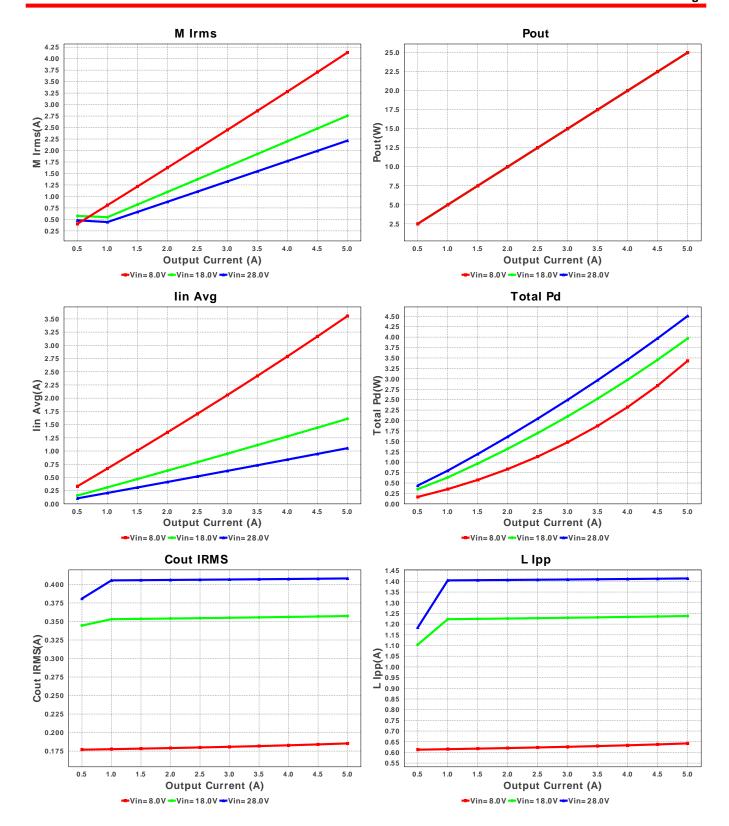

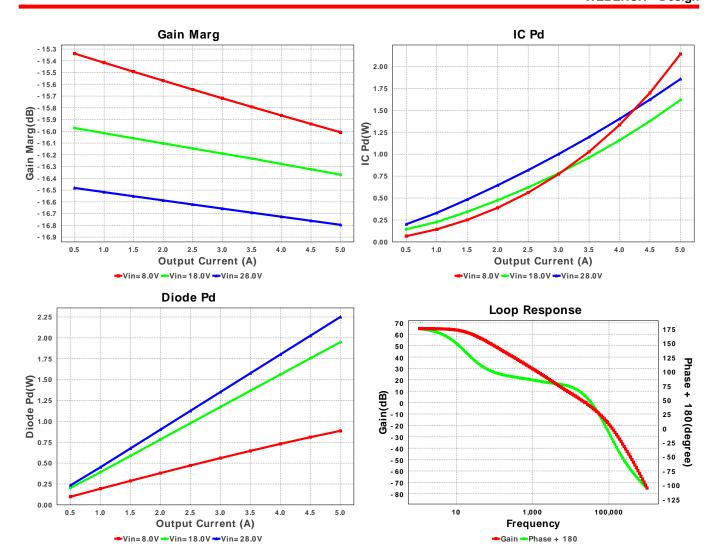

Operating Values

Ope	Operating Values							
#	Name	Value	Category	Description				
1.	Cin IRMS	1.279 A	Current	Input capacitor RMS ripple current				
2.	Cout IRMS	408.094 mA	Current	Output capacitor RMS ripple current				
3.	IC lpk	5.707 A	Current	Peak switch current in IC				
4.	lin Avg	1.054 A	Current	Average input current				
5.	L lpp	1.414 A	Current	Peak-to-peak inductor ripple current				
6.	M1 Irms	2.215 A	Current	Q lavg				
7.	BOM Count	17	General	Total Design BOM count				
8.	FootPrint	309.0 mm ²	General	Total Foot Print Area of BOM components				
9.	Frequency	570.0 kHz	General	Switching frequency				
10.	M Vds Act	220.717 mV	General	Voltage drop across the MosFET				
11.	Pout	25.0 W	General	Total output power				
12.	Total BOM	\$4.26	General	Total BOM Cost				
13.	D1 Tj	131.28 degC	Op_Point	D1 junction temperature				
14.	Vout OP	5.0 V	Op_Point	Operational Output Voltage				
15.	Cross Freq	23.793 kHz	Op_point	Bode plot crossover frequency				
16.	Duty Cycle	19.619 %	Op_point	Duty cycle				
17.	Efficiency	84.723 %	Op_point	Steady state efficiency				
18.	Gain Marg	-18.335 dB	Op_point	Bode Plot Gain Margin				
19.	IC Tj	122.824 degC	Op_point	IC junction temperature				
20.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance				
21.	IOUT_OP	5.0 A	Op_point	lout operating point				
22.	Phase Marg	59.138 deg	Op_point	Bode Plot Phase Margin				
23.	VIN_OP	28.0 V	Op_point	Vin operating point				
24.	Vout p-p	4.381 mV	Op_point	Peak-to-peak output ripple voltage				
25.	Cin Pd	1.635 mW	Power	Input capacitor power dissipation				
26.	Cout Pd	333.082 μW	Power	Output capacitor power dissipation				
27.	Diode Pd	2.251 W	Power	Diode power dissipation				
28.	IC Pd	1.856 W	Power	IC power dissipation				
29.	L Pd	398.75 mW	Power	Inductor power dissipation				
30.	Total Pd	4.508 W	Power	Total Power Dissipation				
31.	Low Freq Gain	64.874 dB	Unknown	Gain at 10Hz				

Design Inputs

#	Name	Value	Description
1.	lout	5.0	Maximum Output Current
2.	lout1	5.0	Output Current #1
3.	VinMax	28.0	Maximum input voltage
4.	VinMin	8.0	Minimum input voltage
5.	Vout	5.0	Output Voltage
6.	Vout1	5.0	Output Voltage #1
7.	base_pn	TPS54531	Base Product Number
8.	source	DC	Input Source Type
9.	Та	30.0	Ambient temperature

Design Assistance

1. TPS54531 Product Folder: http://www.ti.com/product/tps54531: contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to Texas Instruments' Site Terms and Conditions of Use. Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the Evaluation License Agreement.